



DIGITAL DESIGN 2nd LAB

PRELIMINARY REPORT

Course Code: CS 223

Course Name: Digital Design

Section: 1

Name: Arda

Surname: İynem

Student ID: 22002717


Date: 27.02.2022



HALF ADDER

CIRCUIT SCHEMATIC
BEHAVIORAL MODULE
TESTBENCH

(b) Circuit Schematic for Half Adder

 

(g) Behavioral SystemVerilog Module for Half Adder

```
module half_adder(input logic a,b, output logic s,c);  
  assign s = a ^ b;  
  assign c = a & b;  
endmodule
```

(g) Testbench for Half Adder

```
module testbench_half_adder();  
  logic a,b;  
  logic s,c;  
  
  half_adder dut(a,b,s,c);  
  initial begin  
    a = 0; b = 0; #10;  
    b = 1; #10;  
    a = 1; b = 0; #10;  
    b = 1; #10;  
  end  
endmodule
```




HALF SUBTRACTOR

CIRCUIT SCHEMATIC

BEHAVIORAL MODULE

TESTBENCH

 (c) Circuit Schematic for Half Subtractor



'04 5V: 14 GND: 7
'08 5V: 14 GND: 7
'86 5V: 14 GND: 7

(h) Behavioral SystemVerilog Module for Half Subtractor

```
module half_subtractor(input logic a,b,  
                      output logic d,bout);  
  
    assign d = a ^ b;  
    assign bout = ~a & b;  
endmodule
```

(h) Testbench for Half Subtractor

```
module testbench_half_subtractor();  
    logic a,b;  
    logic d,bout;  
  
    half_subtractor dut(a,b,d,bout);  
    initial begin  
        a = 0; b = 0; #10;  
        b = 1; #10;  
        a = 1; b = 0; #10;  
        b = 1; #10;  
    end  
endmodule
```




FULL ADDER (USING HALF ADDERS)

CIRCUIT SCHEMATIC

STRUCTURAL MODULE

TESTBENCH

 (d) Circuit Schematic for Full Adder (Using Half Adders)



(i) Structural SystemVerilog Module for Full Adder (Using Half Adders)

```
module full_adder(input logic a,b,cin,
                  output logic s,cout);
    logic s0, c0, c1;

    half_adder ha(a,b,s0,c0);
    half_adder ha2(s0,cin,s,c1);

    assign cout = c0 | c1;
endmodule
```

(i) Testbench for Full Adder

```
module testbench_full_adder();
    logic a,b,cin;
    logic s,cout;

    full_adder dut(a,b,cin,s,cout);
    initial begin
        a = 0; b = 0; cin = 0; #10;
        cin = 1; #10;
        b = 1; cin = 0; #10;
        cin = 1; #10;
        a = 1; b = 0; cin = 0; #10;
        cin = 1; #10;
        b = 1; cin = 0; #10;
        cin = 1; #10;
    end
endmodule
```




2-BIT ADDER (USING FULL ADDERS)

CIRCUIT SCHEMATIC

STRUCTURAL MODULE

TESTBENCH

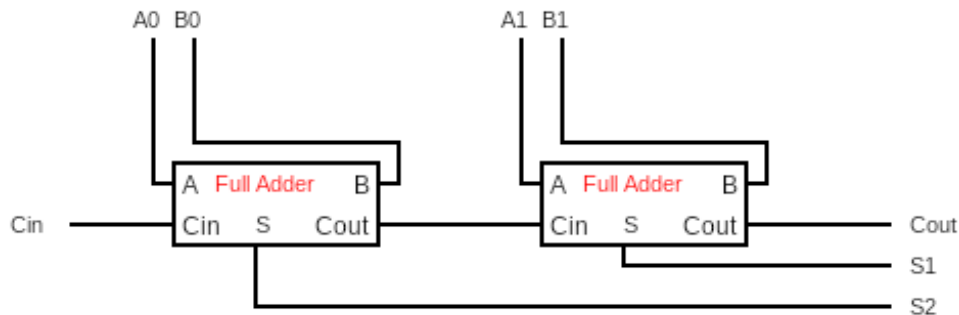(e) Circuit Schematic for 2-Bit Adder (Using Full Adders)



(j) Structural SystemVerilog Module for 2-Bit Adder (Using Full Adders)

```
module two_bit_adder(input logic a0,b0,a1,b1,
                    output logic s0,s1,cout);
    logic cout0;

    full_adder fa(a0,b0,0,s0,cout0);
    full_adder fa2(a1,b1,cout0,s1,cout);
endmodule
```

(j) Testbench for 2-Bit Adder

```
module testbench_two_bit_adder();
    logic a0,b0,a1,b1;
    logic s0,s1,cout;


    two_bit_adder dut(a0,b0,a1,b1,s0,s1,cout);
    initial begin
        a0 = 0; b0 = 0; a1 = 0; b1 = 0; #10;
        b1 = 1; #10;
        a1 = 1; b1 = 0; #10;
        b1 = 1; #10;
        b0 = 1; a1 = 0; b1 = 0; #10;
        b1 = 1; #10;
        a1 = 1; b1 = 0; #10;
        b1 = 1; #10;
        a0 = 1; b0 = 0; a1 = 0; b1 = 0; #10;
        b1 = 1; #10;
        a1 = 1; b1 = 0; #10;
        b1 = 1; #10;
        b0 = 1; a1 = 0; b1 = 0; #10;
        b1 = 1; #10;
        a1 = 1; b1 = 0; #10;
        b1 = 1; #10;
    end
endmodule
```




LAB CALCULATOR

CIRCUIT SCHEMATIC

 (f) Circuit Schematic for Lab Calculator (Using Gates Only)



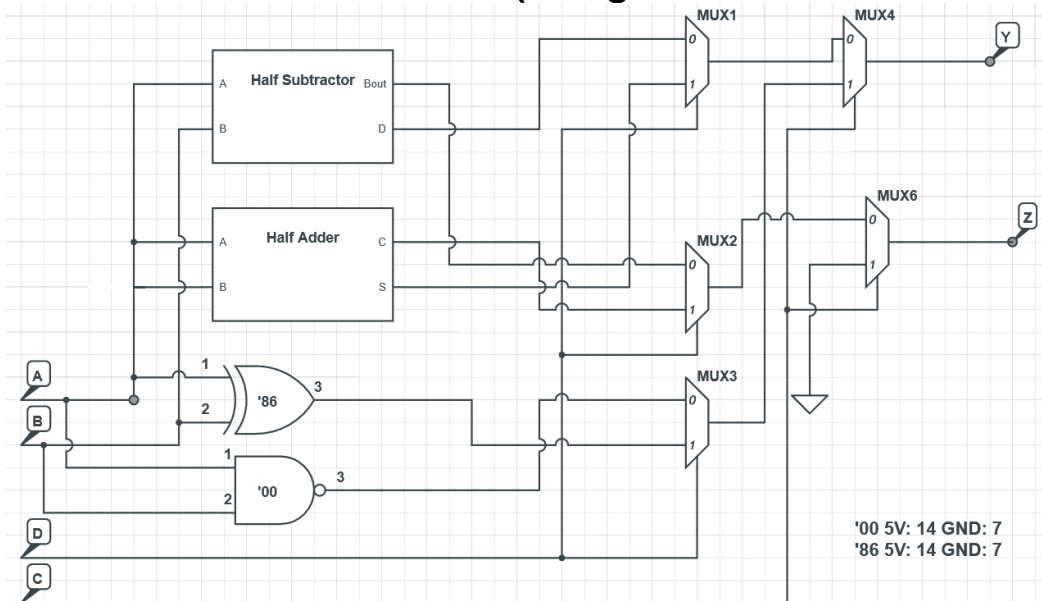(f) Circuit Schematic for Lab Calculator (Using Half Adder/Subtractor and MUX)





LAB CALCULATOR

STRUCTURAL MODULE TESTBENCH

(k) Structural SystemVerilog Module for Lab Calculator (Using Half Adders and Half Subtractors)

```
module lab_calculator(input logic a,b,c,d,
                      output logic y,z);
    logic tmp_s, tmp_cout, tmp_d, tmp_bout;

    half_adder ha(a, b, tmp_s, tmp_cout);
    half_subtractor hs(a, b, tmp_d, tmp_bout);

    assign y = c ? (d ? tmp_d : tmp_s)
                : (d ? ~(a & b) : (a ^ b));
    assign z = c ? (d ? tmp_bout : tmp_cout)
                : (d ? 0 : 0);
endmodule
```

(k) Testbench for Lab Calculator

```
module testbench_lab_calculator();
    logic a,b,c,d;
    logic y,z;

    lab_calculator dut(a,b,c,d,y,z);
    initial begin
        c = 0; d = 0; a = 0; b = 0; #10;
        b = 1; #10;
        a = 1; b = 0; #10;
        b = 1; #10;
        d = 1; a = 0; b = 0; #10;
        b = 1; #10;
        a = 1; b = 0; #10;
        b = 1; #10;
        c = 1; d = 0; a = 0; b = 0; #10;
        b = 1; #10;
        a = 1; b = 0; #10;
        b = 1; #10;
        d = 1; a = 0; b = 0; #10;
        b = 1; #10;
        a = 1; b = 0; #10;
        b = 1; #10;
    end
endmodule
```